

Title:

Physical (Layout) design of Complex Functions for Implementation in Various Target (Implementation) technologies – MPGAs, Full-Custom Chips and CBICs.

Abstraction:

In this experiment we are going to learn how to design Physical layout of complex Function in various technologies like Mask Programmable Gate Arrays, Cell Based Integrated Circuits, Full-Custom chips. We are going to learn how to prepare a transistor level schematic and design complex Boolean Function using complimentary CMOS logic and NAND-NOR network.

Theory and Methodology:

The complimentary CMOS logic implementation of Boolean Function

$$Y = ((A \cdot B) + (C \cdot D))'$$

Logic Level View :



 


Figure 1: Logic Level Schematic of $Y = ((A \cdot B) + (C \cdot D))'$.

Circuit (Transistor) Level View :

 


 

(e)


$Y = ((A \cdot B) + (C \cdot D))'$ designed with 8 transistors—4 PMOS devices and 4 NMOS devices in Full-Custom Design Implementation Technology.

Modified Circuit Diagram :

 

Implementation of Half adder:

Logic Level View :

 

Half adder sum equation is $S = A \oplus B$.

$$= \overline{\overline{A \oplus B}}$$

$$= \overline{\overline{A} \bullet \overline{B} + A \bullet B} \quad \dots\dots\dots (2A1)$$

$$= \overline{A + B + A \bullet B}$$

$$= \overline{A + B + C_{out}} \quad \dots\dots\dots (2A2)$$

$C_{out} = A \bullet B$

$$= \overline{\overline{A \bullet B}} = \overline{\overline{A} + \overline{B}} \quad \dots\dots\dots (2B)$$

Circuit (Transistor) Level View :

Apparatus:

- A Windows-based (XP or 7) PC with standard word processors (i.e. Microsoft Office) and PDF readers (i.e. Adobe Acrobat Reader/Writer, Foxit Reader/Phantom) installed.

Simulation And Measurement:

Complimentary CMOS Logic:

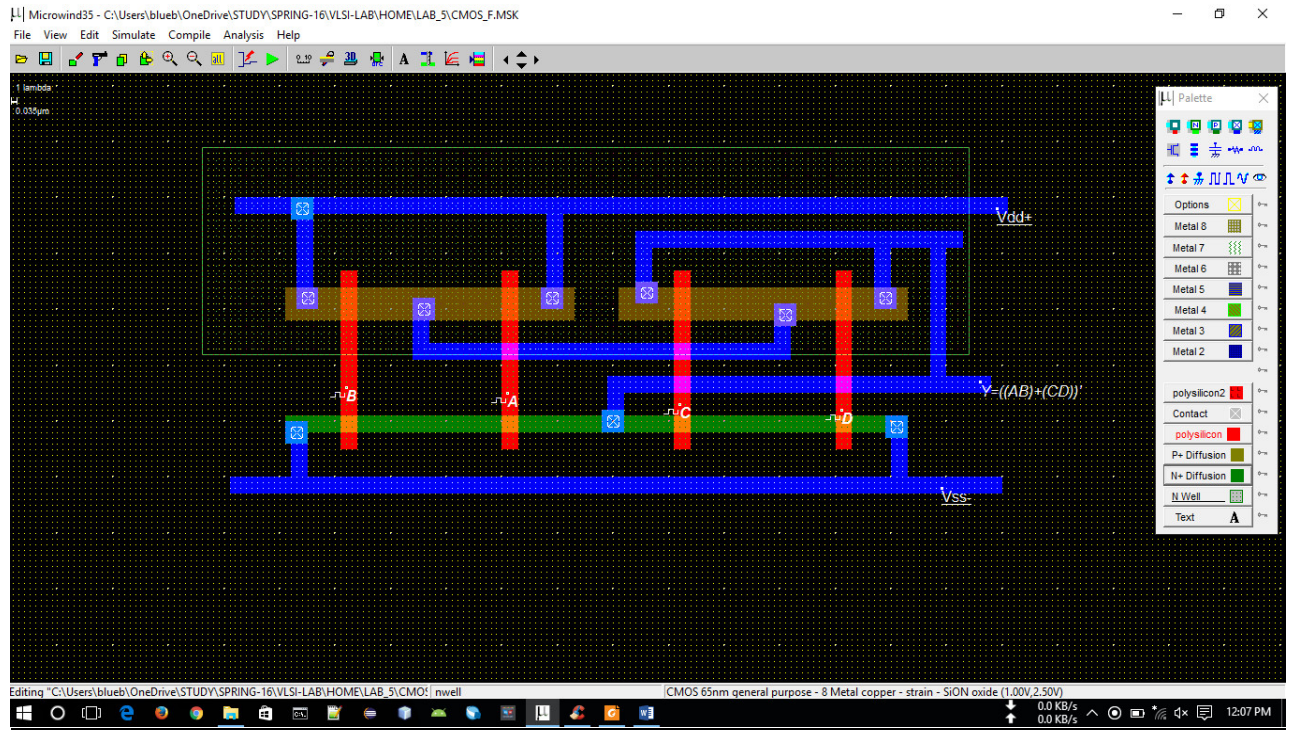


Fig: Complimentary CMOS implementation of $Y = ((A \cdot B) + (C \cdot D))'$

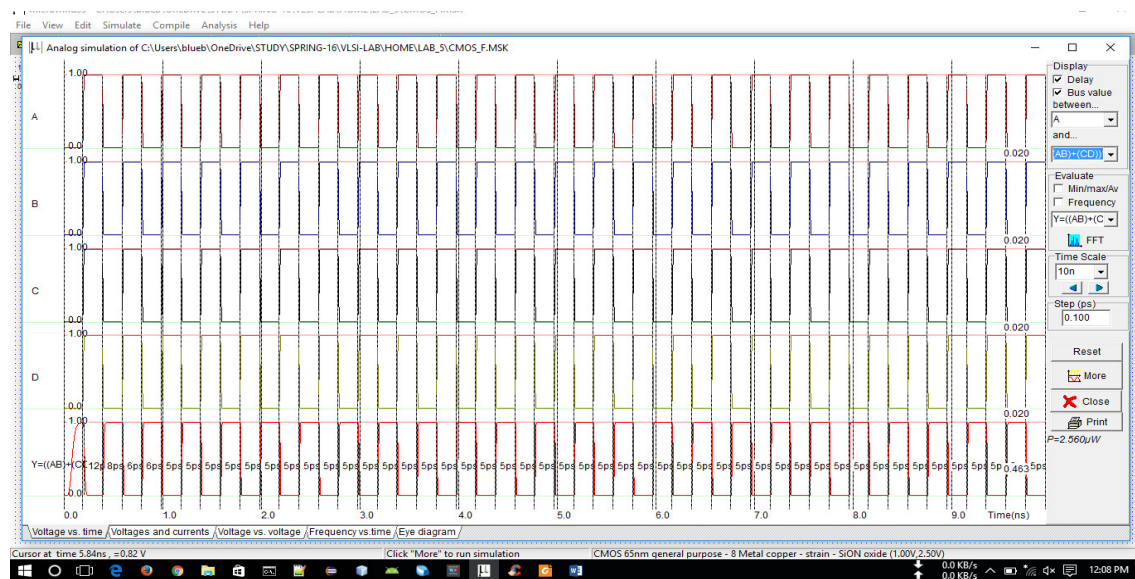


Fig: OUTPUT of $Y = ((A \cdot B) + (C \cdot D))'$

Using NAND-NOR Network:

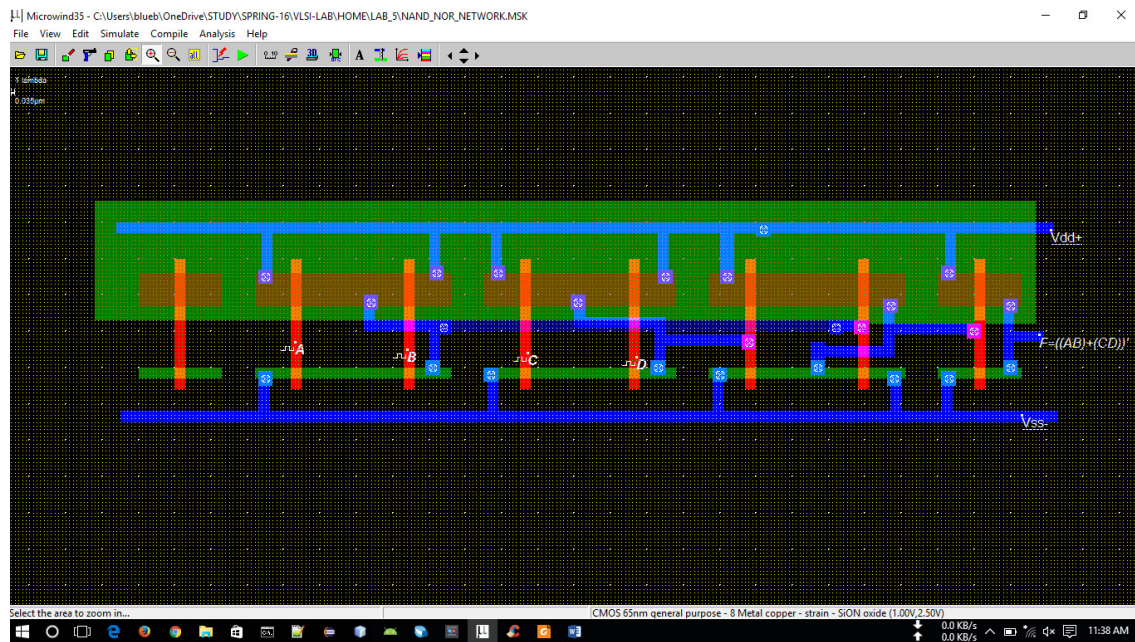


Fig: implementation of $Y = ((A \cdot B) + (C \cdot D))'$ using NAND-NOR Network.

 


Fig: OUTPUT of $Y = ((A \cdot B) + (C \cdot D))'$

NAND-NOR Network implementation of Boolean Function

$$Y = ((A \cdot B) + (C \cdot D))'.$$

Implementing Half Adder Using NOR:

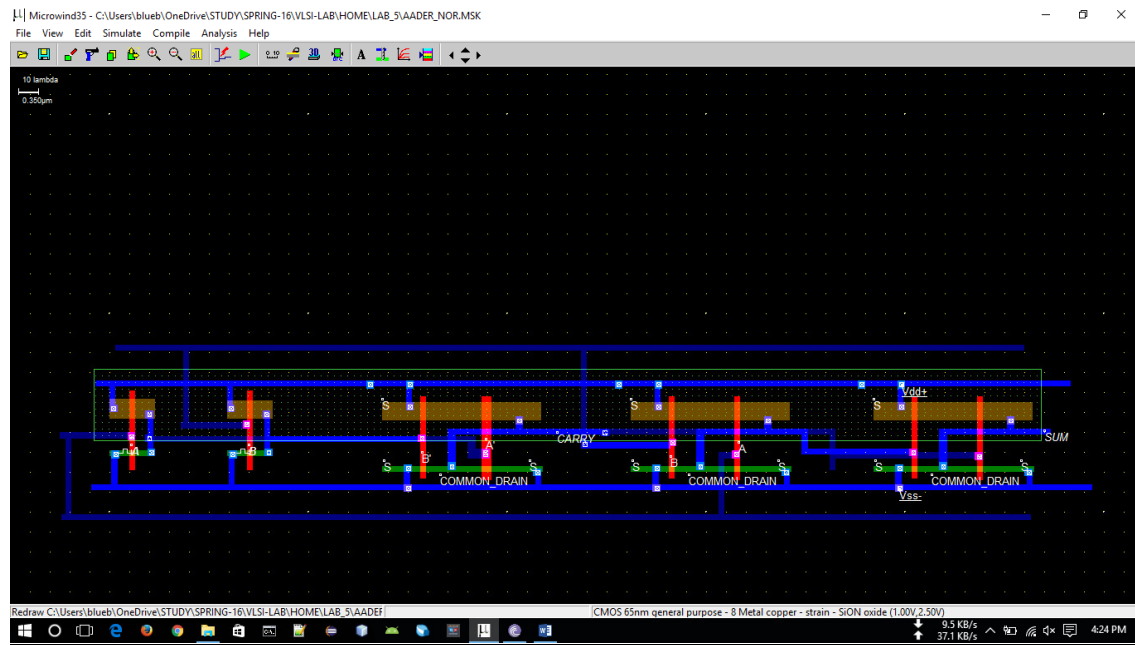


Fig: implementation of Half Adder using NOR.

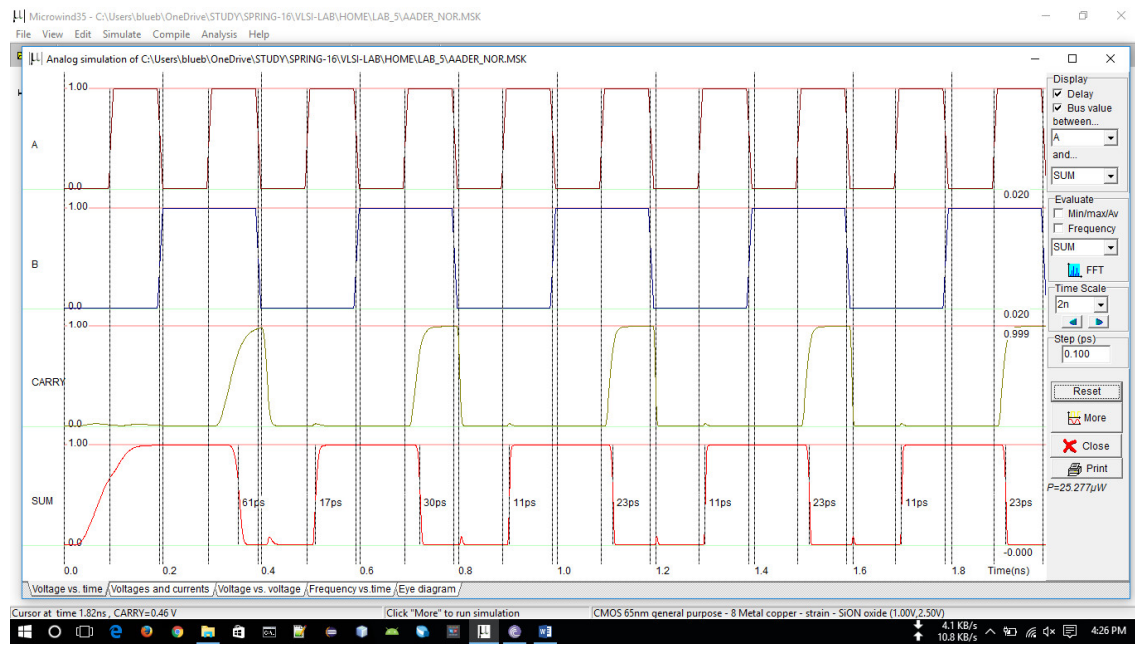


Fig: Output of Half Adder.

Discussion And Conclusion:

In this experiment, we have learnt about how to design Full-custom Chip, implementing Function using complimentary CMOS logic, NAND-NOR network. We also introduced with different type of technologies like- Mask Programmable Gate Array, Cell Based Integrated Circuits.

Reference:

1. R. Jacob Baker, *"CMOS Circuit Design, Layout, and Simulation"*, 3rd Edition, John Wiley & Sons, 2010.
2. John P. Uyemura, *"CMOS Logic Circuit Design"*, Kluwer Academic Publishers, 2002.
3. Etienne Sicard and Sonia Delmas Bendhia, *"Advanced CMOS Cell Design"*, McGraw-Hill, 2007.